

# IÜ 5. Hausübung

## 2.1. Boolische Algebra.

$$a) j(a, b, c, d) = ab + c + \overbrace{\bar{a}\bar{c}d + b\bar{c}d}$$

$$ab + c + \overbrace{\bar{a}\bar{c}d + b\bar{c}d}^{(a+\bar{c})d(\bar{a}+b)}$$

$$ab + c + d(\bar{a}+b)$$

$$ab + c + d\bar{a} + bd = ab + d(\bar{a}+b) + c$$

$$b) k(a, b, c, d) = \overline{\bar{a}b\bar{c}} \cdot \overline{ab\bar{c}}$$

$$(\bar{a} + \bar{b} + \bar{c}) \cdot (\bar{a} + b + \bar{c})$$

$$\bar{a}\bar{b} + ab + ac + \bar{b}\bar{a} + \bar{b}b + \bar{b}c + \bar{a}c + \bar{b}c + bc + \bar{c}c$$

$$c((ab + a\bar{b} + \bar{a} + b + 1) + \bar{b}(b + b) + \bar{a} = \bar{c}(a + \bar{a}) = C$$

$$X + XY = X \text{ норюнгне}$$

$$X + \bar{X}Y = X + Y \text{ ордебан}$$

$$c) l(a, b, c, d) = abc + ab\bar{d} + a\bar{c} + \bar{a}b\bar{c}d + \bar{a}c$$

$$a(bc + bd + \bar{c}) - \bar{a}(\bar{b}\bar{c}d + c)$$

$$a(\underbrace{bc + \bar{c} + bd}_{b + \bar{c} + bd}) - \bar{a}(\underbrace{c + \bar{c}(\bar{b}d)}_{c + \bar{b}d})$$

$$b + \bar{c} + bd$$

$$b + \bar{b}d + \bar{c}$$

$$b(1 + \bar{d}) + \bar{c}$$

$$b + \bar{c}$$

$$a(b + \bar{c})$$

$$ab + ac$$

$$c + \bar{b}d$$

$$\bar{a}((c + \bar{b}d))$$

$$\bar{a}c + \bar{a}\bar{b}d$$

$$d) m(a, b, c, d) = (a + \bar{b} + c) \overline{ab + \bar{a}\bar{c}}$$

$$(\bar{a} + \bar{b})(\bar{a} + \bar{c})$$

$$(\bar{a} + \bar{b}) \cdot (a + c)$$

$$(a + \bar{b} + c)(\bar{a} + \bar{b})(a + c)$$

$$(b + \underbrace{a + c}_{\text{норюнгне}})(a + c)(\bar{a} + b)$$

$$(a + c)(\bar{a} + b)$$

$$a\bar{a} + a\bar{b} + c\bar{a} + c\bar{b}$$

$$a\bar{a} = 0$$

$$0 + a\bar{b} + c\bar{a} + cb$$

$$a\bar{b} + c\bar{a} + cb$$

$$a\bar{b} + b\bar{c} + c\bar{a}$$

$$ab + ca$$

$$XY + \bar{X}Z + YZ = XY + \bar{X}Z$$

могена консекуя  
склеиване

2.1. b)  $j(a, b, c, d)$

$$\begin{array}{cccc|ccccc} \text{Jimpl: } & ab + c + \bar{a}d + bd & = ab + c + \bar{a}\bar{c}d + b\bar{c}d = j_{\text{orig}} \\ a & b & c & d & ab & c & \bar{a}cd & bc\bar{d} & j_{\text{orig}} \\ 0 \rightarrow & & & & 0 & & 0 & 0 & \\ 0 \rightarrow & & & & 0 & & 0 & 0 & \\ & | & | & | & | & | & | & | & \\ & | & | & | & | & | & | & | & \\ & | & | & | & | & | & | & | & \\ \text{U.SW.} & & & & & & & & \end{array}$$

Viel zu viel

$$\begin{aligned} c) \quad j = & \bar{a}\bar{b}\bar{c}\bar{d} + \bar{a}\bar{b}\bar{c}d + \bar{a}\bar{b}cd + \bar{a}\bar{b}\bar{c}\bar{d} + \bar{a}\bar{b}cd + \bar{a}\bar{b}c\bar{d} + \bar{a}\bar{b}\bar{c}d + \\ & + \bar{a}\bar{b}cd + \bar{a}\bar{b}\bar{c}d + \bar{a}\bar{b}c\bar{d} + \bar{a}\bar{b}\bar{c}\bar{d} + \bar{a}\bar{b}cd = \text{KDNF} \\ (\rightarrow & c(a+\bar{a})(b+\bar{b})(d+\bar{d})) \quad \text{quinnomnig na } (x+x) \end{aligned}$$

2.2. Проверка загара.

$$KDNF = M_{SeSr} + M_{Se\bar{Sr}} + M_{\bar{Se}Sr} + M_{\bar{Se}\bar{Sr}}$$

$$m_e = M_{Sr}(Se + \bar{Se}) + M_{\bar{Sr}}(\bar{Se} + Se)$$

$$= M_{Sr} \cdot 1 + M_{\bar{Sr}} \cdot 1$$

$$= M_{Sr} + M_{\bar{Sr}}$$

$$m_e = M_{Sr} + M_{\bar{Sr}}$$

$$m_e = M \oplus Sr$$

$$\begin{array}{c} M \\ \bar{Sr} \\ M \\ \bar{Sr} \end{array} \begin{array}{c} =1 \\ - \\ =1 \\ - \end{array} \begin{array}{c} m_e \text{ лебо} \\ m_r \text{ Трабо} \end{array}$$

$$M_{Sr} + M_{\bar{Sr}} = M(Sr + \bar{Sr}) = M \quad ?!$$

$$\text{Наконе } m_r = M_{Sr} + M_{\bar{Sr}} \quad m_r = M \oplus Sr$$

2.3. Консенсус-Гleichung

$$xy + \bar{x}z + yz = xy + \bar{x}z$$

y21

$$yzx + yzx$$

$$xy + xz + xy2 + \bar{x}y2$$

$$(xy + xy2) + (\bar{x}z + \bar{x}y2)$$

$$xy + \bar{x}z$$

$$\text{Итого: } xy + xz = xy + \bar{x}z$$

4.2.2.  $m_e = 1 \} \begin{cases} \text{links} \\ \text{an} \\ m_r = 1 \end{cases}$  } Motor / Kette       $m_e = 0 \} \begin{cases} \text{anti-} \\ \text{rechts} \\ m_r = 0 \end{cases}$  } aus

$$\left( \frac{m_r}{m_e} \right) = \text{nyuado}$$

$S_e = 1 \} \begin{cases} \text{Seite: Objekt} \\ S_r = 1 \end{cases}$  } curvora       $S_e = 0 \} \begin{cases} \text{Seite: keinen Objekt} \\ S_r = 0 \end{cases}$

$M = 0 \} \begin{cases} \text{Modi (Modus)} \\ M = 1 \end{cases}$  } wegobams zu  
wegobams - breiga bneiegnowa ke raiyan

ser upolambeen - nuborom

oda = ornabamsi ondams

II право :  $m_r = 1, m_e = 1$       II право :  $m_r = 1, m_e = 0$  (mon =  $m_r = 0, m_e = 0$ )

$M = 0$  = wegobams       $S_r, S_e = 0$  - nyuado ( $m_r, m_e = 1$ )

$S_r = 0, S_l = 1$  = O. curva       $m_r = 1, m_e = 0$  n. bueko

$S_e = 0, S_r = 1$  O. curva       $m_r = 0, m_e = 1$  n. bueko

$S_e, S_r = 1$  obzern nyuado       $m_{l,r} = 0$  ongams

a)

M	$S_L$	$S_r$	$m_L$	$m_r$
0	0	0	0	0
0	0	1	1	0
0	1	0	0	1
0	1	1	1	1
1	0	0	1	1
1	0	1	1	1
1	1	0	0	1
1	1	1	0	0

KDNF =  $\langle 1 \rangle \wedge m_e \wedge m_r$

KDNF  $m_e$  :  $\overline{S_L} \overline{S_r} \overline{m_L} \overline{m_r}$

$m_e = (\bar{M} \bar{S}_L \bar{S}_r) + (\bar{M} S_L \bar{S}_r) + (M \bar{S}_L \bar{S}_r) + (M S_L \bar{S}_r)$

KDNF  $m_r$   $010 = (\bar{M} S_L \bar{S}_r) + (M S_L S_r) + (M \bar{S}_L \bar{S}_r) + (M \bar{S}_L S_r)$

$$= \bar{M} S_L \bar{S}_r + M S_L S_r + M \bar{S}_L \bar{S}_r + M \bar{S}_L S_r$$

$$\bar{M} S_r (\bar{S}_L + S_L) + M \bar{S}_r (\bar{S}_L + S_L)$$

$$M S_r + M \bar{S}_r$$

$$M (S_r + \bar{S}_r)$$

$$M$$



$$m_r = \bar{M} S_L \bar{S}_r + M S_L S_r + M \bar{S}_L \bar{S}_r + M S_L \bar{S}_r$$

$$\bar{M} S_L (\bar{S}_r + S_r) + M \bar{S}_L (\bar{S}_r + S_r)$$

$$M S_L + M \bar{S}_L$$

$$M (S_L + \bar{S}_L)$$

$$M$$